

## 第 6 講: BJT 電晶體共射(Common Emitter)放大電路分析

參考文獻與網頁:

- [1]蕭敏學，大學電子學實習(一):電子電路分析篇，台科大圖書，2013
- [2] YouTube: 吳順德，應用電子電實驗(L8 2 戴維寧等效電路在 BJT 分析的應用)  
<https://www.youtube.com/watch?v=kzIOvQeVfYA&list=PLXxs-fSMcpYfBBswuFSBfefLbeBmOUbZ2&index=23>
- [3] How To Calculate The Voltage Gain of a Transistor Amplifier ,  
<https://www.youtube.com/watch?v=-MyVscG-Pew>
- [4]Basic BJT Amplifiers,  
<http://cdcpc.ce.ncu.edu.tw/classes/EEShortversion/Elect/Ch6%20Basic%20BJT%20Amplifiers.pdf>

一、電路分析，請參考[1]~[3]

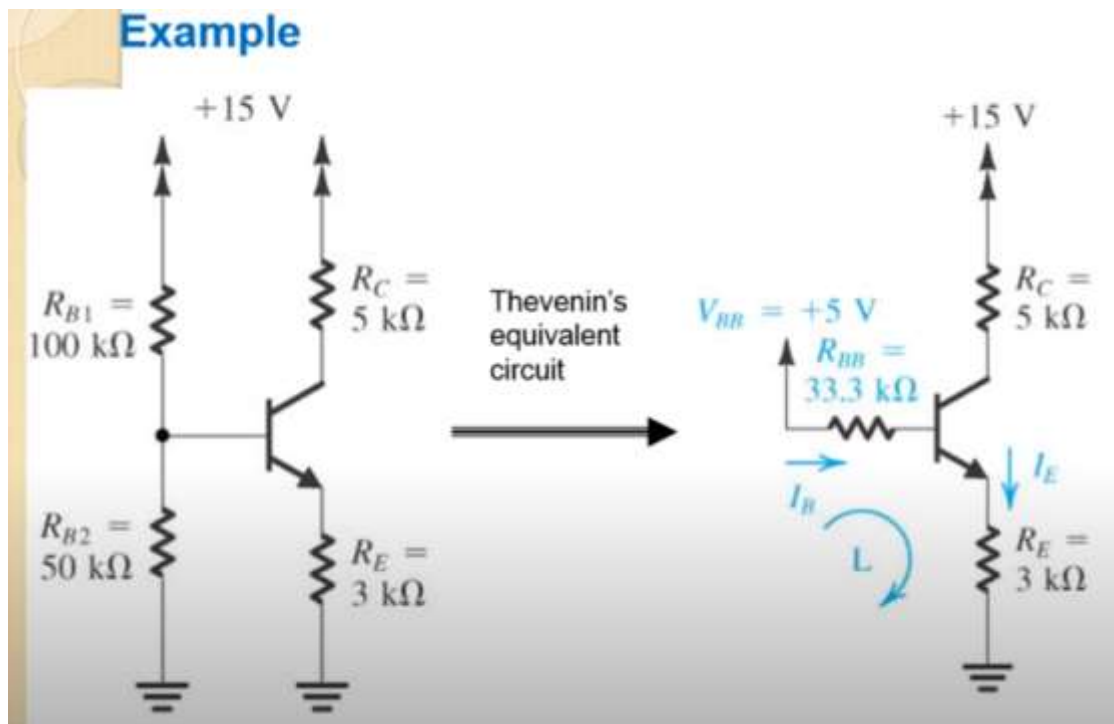


圖 6-1 BJT 電晶體共射電路之等效電路

$$R_{BB} = R_{B1} // R_{B2} = 100\text{K} // 50\text{K} = 33.3 \text{ K}$$

$$V_{BB} = V_{CC} * \frac{R_{B2}}{R_{B1} + R_{B2}} = 15 * \frac{50}{100 + 50} = 5 \text{ V}$$

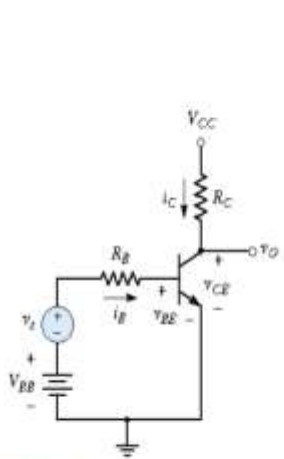


Figure 4.3 A common-emitter circuit with time-varying signal source in series with the base dc source

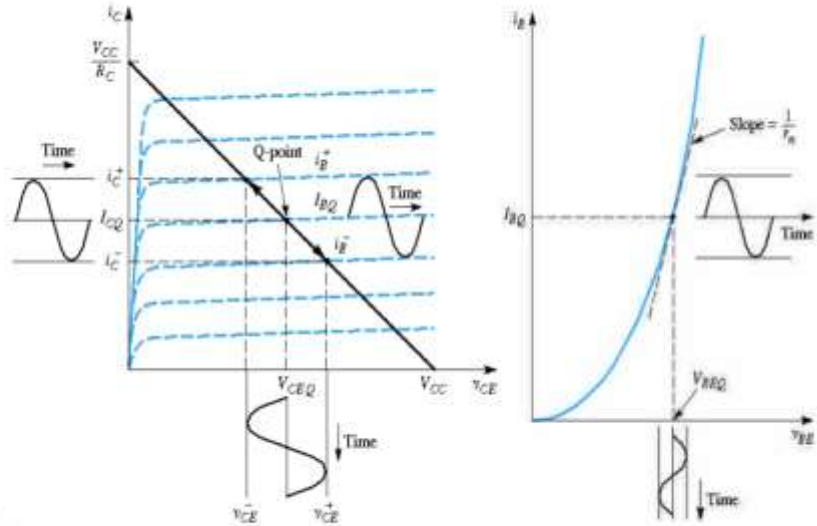


Figure 4.4 Common-emitter transistor characteristics, dc load line, and sinusoidal variation in base current, collector current, and collector-emitter voltage

圖 6-2 共射電路[4]


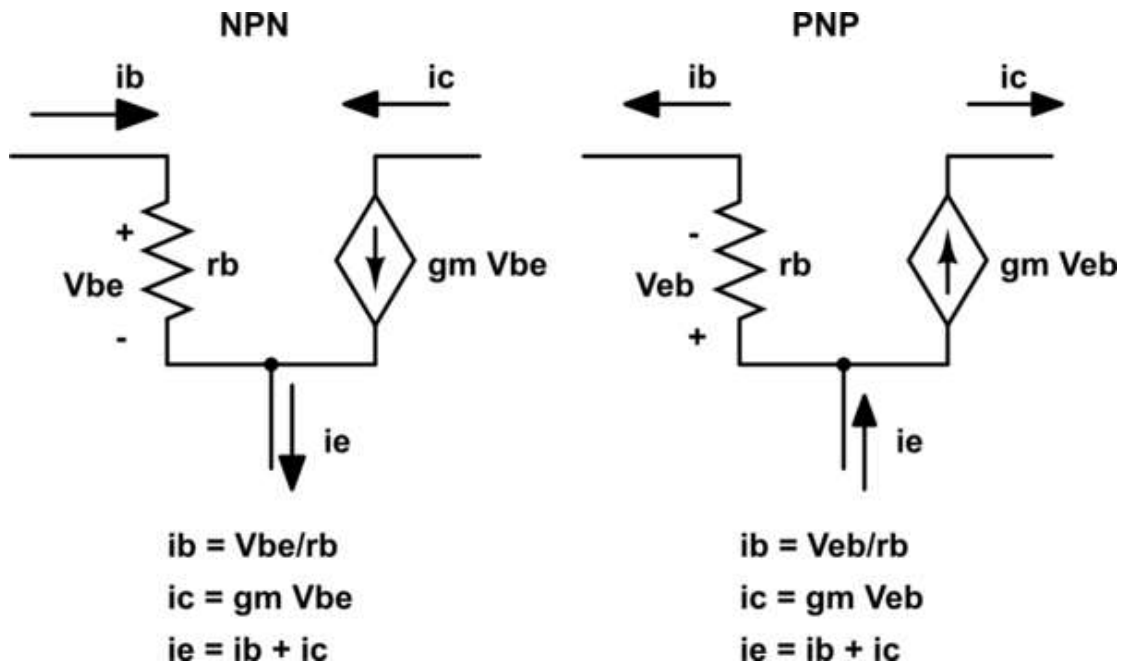


圖 6-3 NPN and PNP BJT Transistor hybrid  $\pi$  models,  $r_b = r_{\pi}$  (sometimes using)

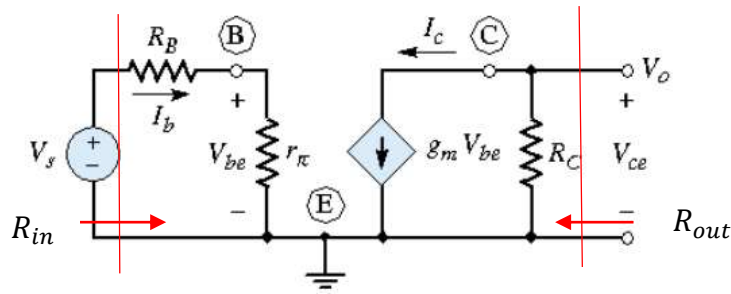

**Figure 4.11** The small-signal equivalent circuit of the common-emitter circuit using the npn transistor hybrid- $\pi$  model

$$V_o = -g_m V_{be} R_C$$

$$V_o = -\beta I_b R_C$$

$$V_{be} = \left( \frac{r_\pi}{r_\pi + R_B} \right) V_s$$

$$I_b = \frac{V_s}{r_\pi + R_B}$$

$$A_v = \frac{V_o}{V_s} = -g_m R_C \frac{r_\pi}{r_\pi + R_B}$$

$$A_v = \frac{V_o}{V_s} = -\frac{\beta R_C}{r_\pi + R_B}$$

圖 6-4 共射電路小訊號模型[4]

$$\text{輸入電阻} = R_{in} = \frac{V_s}{i_b} = \frac{i_b(R_B + r_\pi)}{i_b} = R_B + r_\pi$$

$$\text{輸出電阻} = R_{out} = R_C$$

$$\text{電壓放大率} = A_v = \frac{V_o}{V_s} = \frac{-i_c R_{out}}{i_b R_{in}} = \frac{-\beta R_{out}}{R_{in}} = -\frac{\beta R_C}{R_B + r_\pi}$$

$$\text{BE 導通電阻 } r_b = r_\pi = \frac{\beta V_T}{I_{CQ}}, \quad V_T = 0.026, \quad I_{CQ} = \text{Q-point } I_c$$

$$\text{電流放大率} = \beta = \frac{i_c}{i_b} = \frac{g_m V_{be}}{V_{be}/r_\pi} = g_m * r_\pi$$

● 共射電路小訊號放大電路範例 1 [4]

**Example 4.1 Objective:** Calculate the small-signal voltage gain of the bipolar transistor circuit shown in Figure 4.3.

Assume the transistor and circuit parameters are:  $\beta = 100$ ,  $V_{CC} = 12\text{ V}$ ,  $V_{BE} = 0.7\text{ V}$ ,  $R_C = 6\text{ k}\Omega$ ,  $R_B = 50\text{ k}\Omega$ , and  $V_{BB} = 1.2\text{ V}$ .

**DC Solution:** We first do the dc analysis to find the  $Q$ -point values. We obtain

$$I_{BQ} = \frac{V_{BB} - V_{BE(\text{on})}}{R_B} = \frac{1.2 - 0.7}{50} \Rightarrow 10\ \mu\text{A}$$

so that

$$I_{CQ} = \beta I_{BQ} = (100)(10\ \mu\text{A}) \Rightarrow 1\text{ mA}$$

Then,

$$V_{CEQ} = V_{CC} - I_{CQ}R_C = 12 - (1)(6) = 6\text{ V}$$

Therefore, the transistor is biased in the forward-active mode.

**AC Solution:** The small-signal hybrid- $\pi$  parameters are

$$r_\pi = \frac{\beta V_T}{I_{CQ}} = \frac{(100)(0.026)}{1} = 2.6\text{ k}\Omega$$

and


$$g_m = \frac{I_{CQ}}{V_T} = \frac{1}{0.026} = 38.5\text{ mA/V}$$

The small-signal voltage gain is determined using the small-signal equivalent circuit shown in Figure 4.11. From Equation (4.23), we find

$$A_v = \frac{V_o}{V_s} = -(g_m R_C) \cdot \left( \frac{r_\pi}{r_\pi + R_B} \right)$$

or
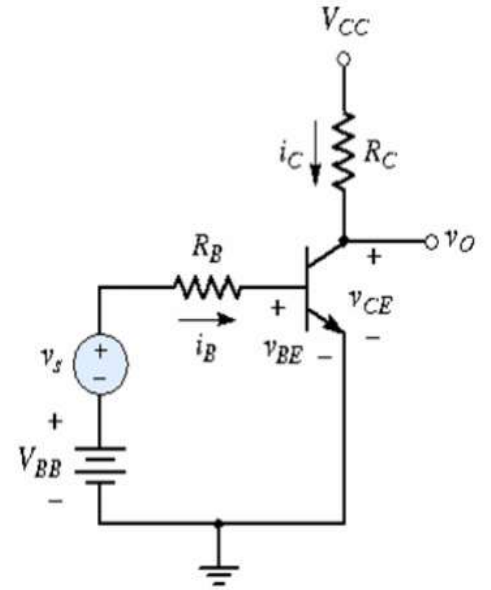
$$= -(38.5)(6) \left( \frac{2.6}{2.6 + 50} \right) = -11.4$$



● 共射電路小訊號放大電路範例 2 [4]

**Example 4.4 Objective:** Determine the small-signal voltage gain of the circuit shown in Figure 4.25.

Assume the transistor parameters are:  $\beta = 100$ ,  $V_{BE(on)} = 0.7V$ , and  $V_A = 100V$ .

A. DC analysis

$$V_{th} = \frac{6.3}{93.7 + 6.3} \times 12 = 0.756V$$

$$R_{th} = 93.7K // 6.3K = 5.9K$$

$$I_{BQ} = I_B = \frac{0.756 - 0.7}{5.9K} = 9.5\mu A$$

$$I_{CQ} = I_C = 100I_B = 0.95mA$$

B. AC analysis

$$r_{\pi} = \frac{\beta V_T}{I_{CQ}} = 100 \times \frac{0.026}{0.95} \times 10^3 = 2.736K$$

$$r_o = \frac{V_A}{I_{CQ}} = \frac{100}{0.95} \times 10^3 = 105K$$

$$i_b = \frac{v_{\pi}}{r_{\pi}} = \frac{1}{r_{\pi}} \times \frac{6.3 // 93.7 // r_{\pi}}{6.3 // 93.7 // r_{\pi} + 0.5} v_s = 0.288v_s$$

$$v_o = -\beta i_b \times (r_o // R_C) = -100 \times 0.288v_s \times 5.67 = -163.23v_s$$

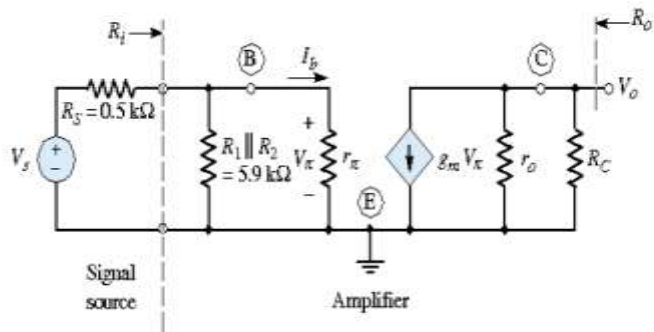
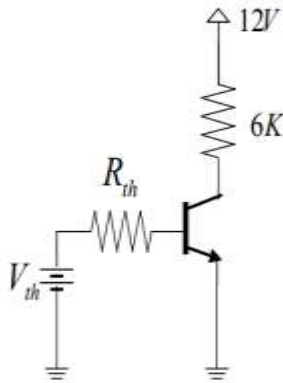
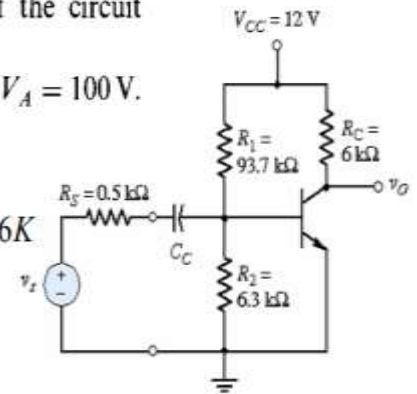


Figure 4.26 The small-signal equivalent circuit, assuming the coupling capacitor is a short circuit

● 共射電路小訊號放大電路範例 3 [4]

**Example 4.5 Objective:** Determine the small-signal voltage gain of a common-emitter circuit with an emitter resistor.

For the circuit in Figure 4.28, the transistor parameters are:  $\beta = 100$ ,  $V_{BE(on)} = 0.7V$ , and  $V_A = \infty$ .


A. DC analysis

$$V_{th} = \frac{12.2}{56 + 12.2} \times 10 = 1.79V$$

$$R_{th} = 56K // 12.2K = 10K$$

$$I_B = \frac{1.79 - 0.7}{10 + (1 + 100) \times 0.4} = 0.0216mA$$

$$I_C = 100I_B = 2.16mA$$

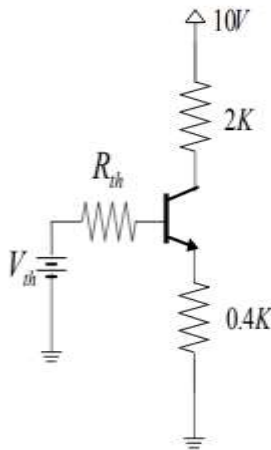

B. AC analysis

$$r_{\pi} = \frac{\beta V_T}{I_{CQ}} = 100 \times \frac{0.026}{2.16} = 1.2K$$

$$i_s = \frac{v_s}{10 // (r_{\pi} + (1 + \beta) \times 0.4) + 0.5} = 0.1168v_s, mA$$

$$i_b = \frac{10}{10 + (r_{\pi} + (1 + \beta) \times 0.4)} \times i_s = 0.1938i_s, mA$$

$$v_o = -\beta i_b \times R_C = -100 \times 0.1938 \times 0.1168v_s \times 2 = -4.527v_s$$

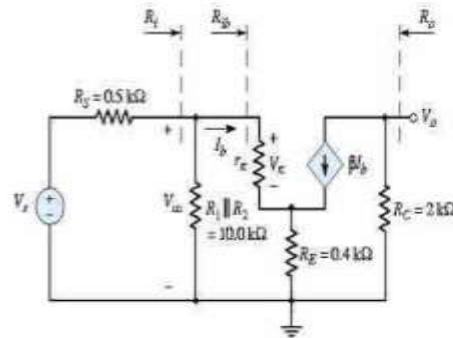
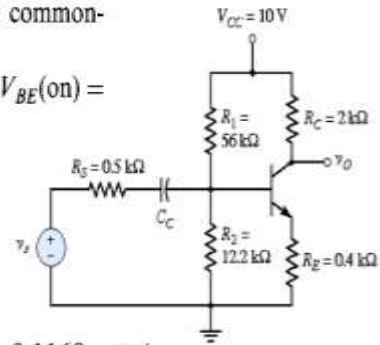


Figure 4.29 The small-signal equivalent circuit with an emitter resistor

The input resistance to the amplifier is now

$$R_i = R_1 // R_2 // R_{th} \quad (4.48)$$

We can again relate  $V_{in}$  to  $V_s$  through a voltage-divider equation as

$$V_{in} = \left( \frac{R_i}{R_i + R_S} \right) \cdot V_s \quad (4.49)$$

Combining Equations (4.45), (4.47), and (4.49), we find the small-signal voltage gain is

$$A_v = \frac{V_o}{V_s} = \frac{-(\beta I_b) R_C}{V_s} = -\beta R_C \left( \frac{V_{in}}{R_{th}} \right) \cdot \left( \frac{1}{V_s} \right) \quad (4.50(a))$$

or

$$A_v = \frac{-\beta R_C}{r_{\pi} + (1 + \beta) R_E} \left( \frac{R_i}{R_i + R_S} \right) \quad (4.50(b))$$

From this equation, we see that if  $R_i \gg R_S$  and if  $(1 + \beta) R_E \gg r_{\pi}$ , then the small-signal voltage gain is approximately

$$A_v \cong \frac{-\beta R_C}{(1 + \beta) R_E} \cong \frac{-R_C}{R_E} \quad \dots \text{independent of } \beta \quad (4.51)$$



- 共射電路小訊號放大電路範例 4 [4]

## Common Emitter Circuit with Emitter Bypass Capacitor

| We can use an emitter bypass capacitor to effectively short out a portion or all of the emitter resistance to enhance the small-signal voltage gain.


**Design Example 4.6 Objective:** An amplifier with the configuration in Figure 4.32 is to be designed such that a 12 mV sinusoidal signal from a microphone is amplified to a 0.4 V sinusoidal output signal. Standard resistor values are to be used in the final design.

**Initial Design Approach:** The magnitude of the voltage gain of the amplifier needs to be

$$|A_v| = \frac{0.4 \text{ V}}{12 \text{ mV}} = 33.3$$

From Equation (4.51), the approximate voltage gain of the amplifier is

$$|A_v| \cong \frac{R_C}{R_{E1}}$$

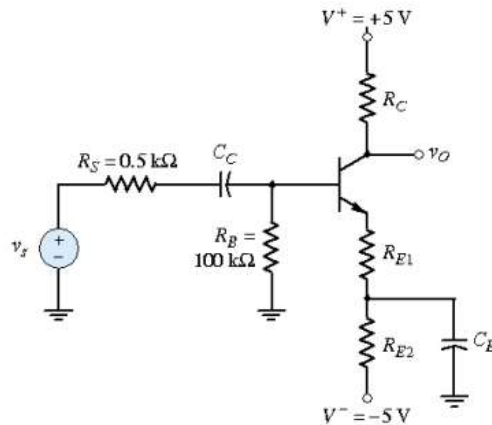

Noting from the last example that this value of gain produces an optimistically high value, we can set  $R_C/R_{E1} = 40$  or  $R_C = 40R_{E1}$ .

The dc base-emitter loop equation is

$$5 = I_B R_B + V_{BE(\text{on})} + I_E (R_{E1} + R_{E2})$$

Assuming  $\beta = 100$  and  $V_{BE(\text{on})} = 0.7 \text{ V}$ , we can design the circuit to produce a quiescent emitter current of, for example, 0.20 mA. We then have

$$5 = \frac{(0.20)}{(101)}(100) + 0.70 + (0.20)(R_{E1} + R_{E2})$$

which yields

$$R_{E1} + R_{E2} = 20.5 \text{ k}\Omega$$

Assuming  $I_E \cong I_C$  and designing the circuit such that  $V_{CEQ} = 4\text{ V}$ , the collector-emitter loop equation produces

$$5 + 5 = I_C R_C + V_{CEQ} + I_E (R_{E1} + R_{E2}) = (0.2)R_C + 4 + (0.2)(20.5)$$

or

$$R_C = 9.5\text{ k}\Omega$$

Then

$$R_{E1} = \frac{R_C}{40} = \frac{9.5}{40} = 0.238\text{ k}\Omega$$

and  $R_{E2} = 20.3\text{ k}\Omega$ .

From Appendix D, we can pick standard resistor values of  $R_{E1} = 240\ \Omega$ ,  $R_{E2} = 20\text{ k}\Omega$ , and  $R_C = 10\text{ k}\Omega$ .

- 結論:

BJT 電晶體共射放大電路、等效電路與小訊號模型如圖 6-5-1, 6-5-2, 6-5-3 所示，

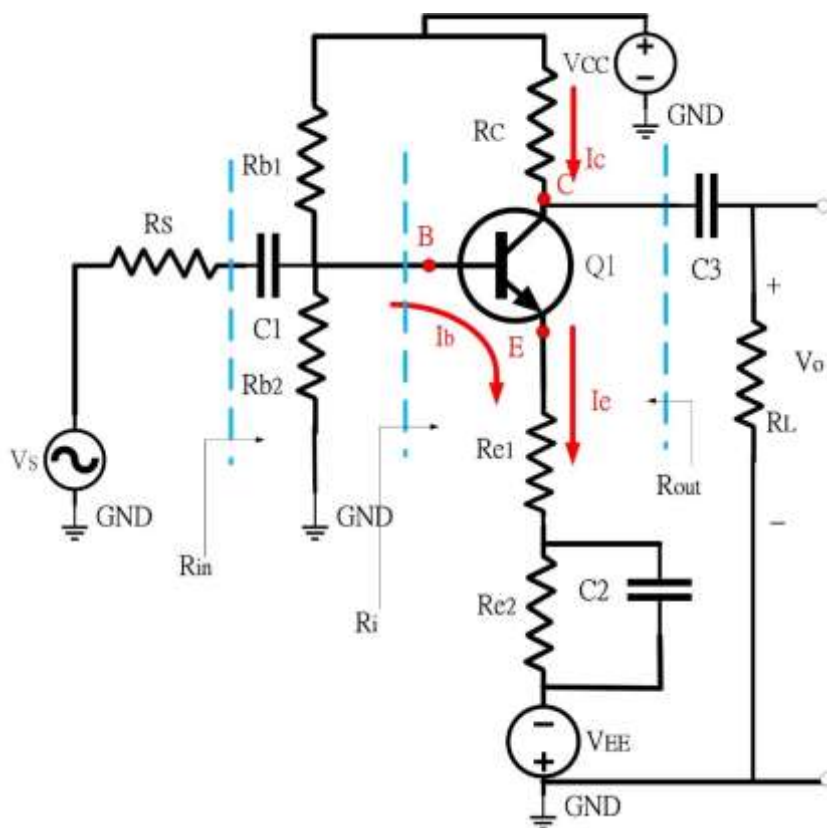


圖 6-5-1 BJT 電晶體共射放大電路



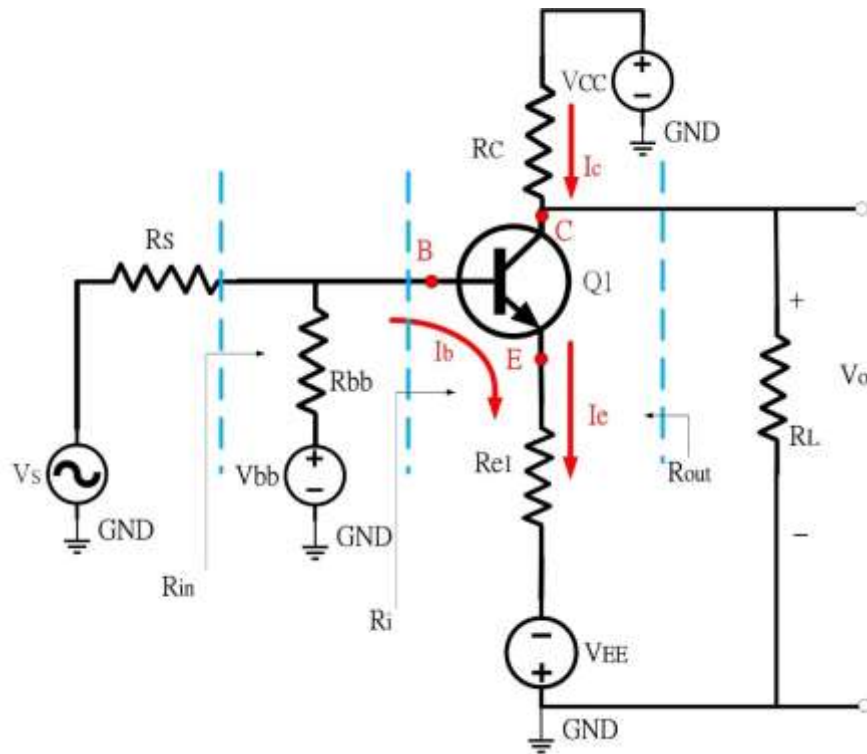


圖 6-5-2 等效電路

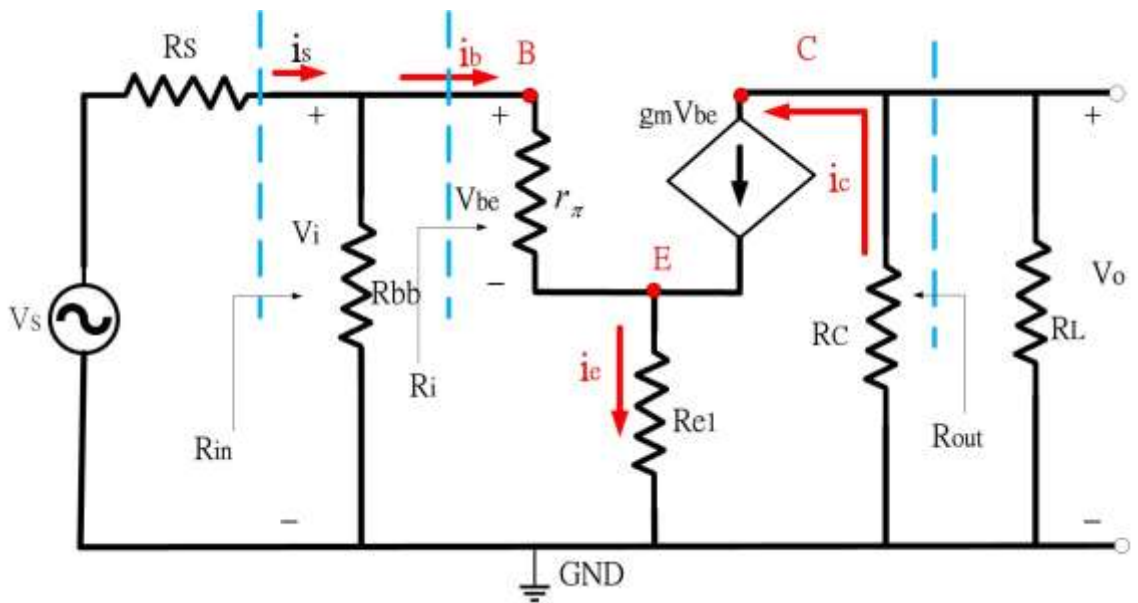


圖 6-5-3 小訊號模型

其中，流經電晶體三極的電流( $I_b, I_c, I_e$ )與偏壓電流( $I_{BQ}, I_{CQ}, I_{EQ}$ )及訊號電流( $i_b, i_c, i_e$ )關係如(6.1)所示:

$$1) \quad I_b = I_{BQ} + i_b, \quad I_c = I_{CQ} + i_c, \quad I_e = I_{EQ} + i_e, \quad (6.1)$$

$$2) \quad \text{電流放大率} \Rightarrow \beta = \frac{I_{CQ}}{I_{BQ}} = \frac{g_m * V_{be}}{V_{be}/r_\pi} = g_m * r_\pi \quad (6.2)$$

$$3) \quad \text{BE 間導通電阻} \quad r_b = r_\pi = \frac{\beta V_T}{I_{CQ}}, \quad V_T = 0.026, \quad I_{CQ} = \text{Q-point } I_c \quad (6.3)$$

$$R_{bb} = R_{b1} // R_{b2}$$

$$4) \quad \text{輸入電阻} \Rightarrow R_{in} = \frac{V_i}{i_s} = R_{bb} // (r_\pi + (1 + \beta)R_{e1}) \\ \cong r_\pi + (1 + \beta)R_{e1} = R_i \quad (6.4)$$

$$5) \quad \text{輸出電阻} \Rightarrow R_{out} = R_C \quad (6.5)$$

$$6) \quad \text{電壓放大率} \Rightarrow A_v = \frac{V_o}{V_s} = \frac{V_o}{V_i} * \frac{V_i}{V_s} = \frac{-i_c * R_C}{i_b * (r_\pi + (1 + \beta)R_{e1})} * \frac{R_{in}}{R_{in} + R_s} \\ = \frac{-\beta * R_C}{r_\pi + (1 + \beta)R_{e1}} * \frac{R_{in}}{R_{in} + R_s} \cong -\frac{R_C}{R_{e1}} * \frac{R_{in}}{R_{in} + R_s} \quad (6.6)$$

例題 5: 考量圖 6-6-1

- 找出 Q-point 的  $V_{CEQ}$ 、 $I_{BQ}$  與  $I_{CQ}$ ， $\beta = I_{CQ} / I_{BQ} = ?$
- 計算  $A_v = ?$  比較理論值與模擬電路輸出入  $V_{p-p}$  波形比率值。
- 計算輸出入電阻  $R_{in}$ 、 $R_{out}$ ，並修改該模擬圖 6-6 驗證該輸出入電阻計算值是否相近。

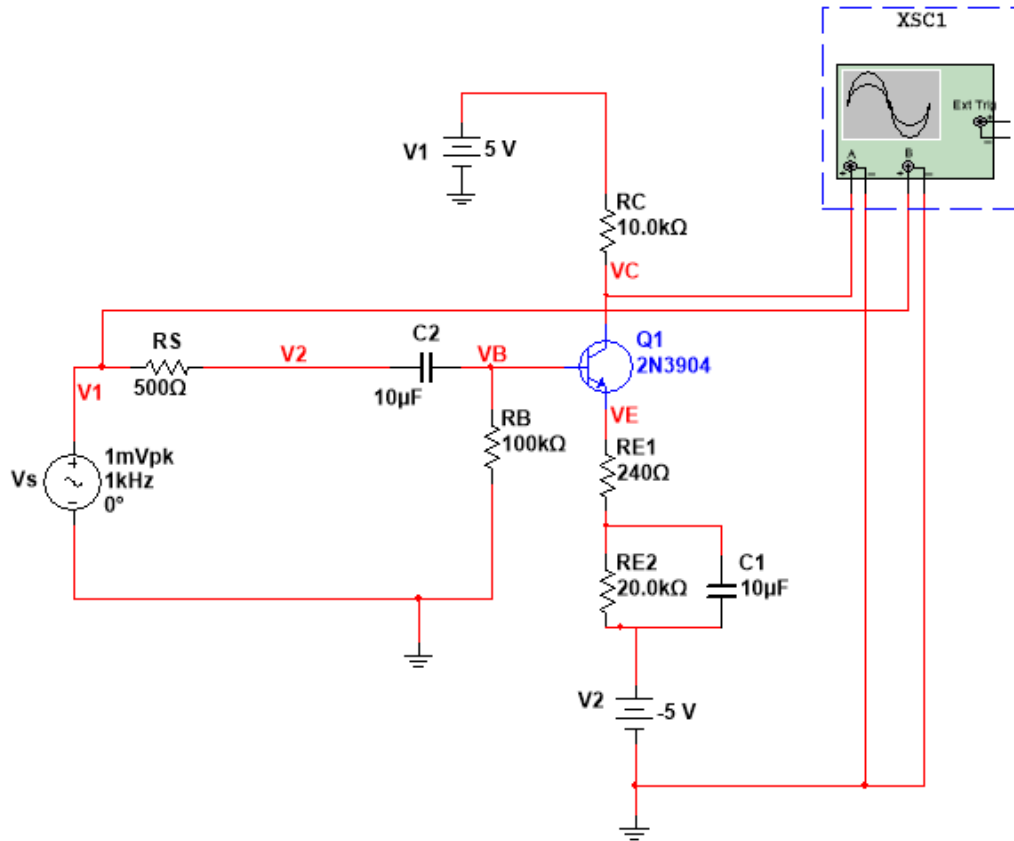


圖 6-6-1

- 使用 Simulate → Analyses → DC operating point，顯示 Q-point 電壓與電流

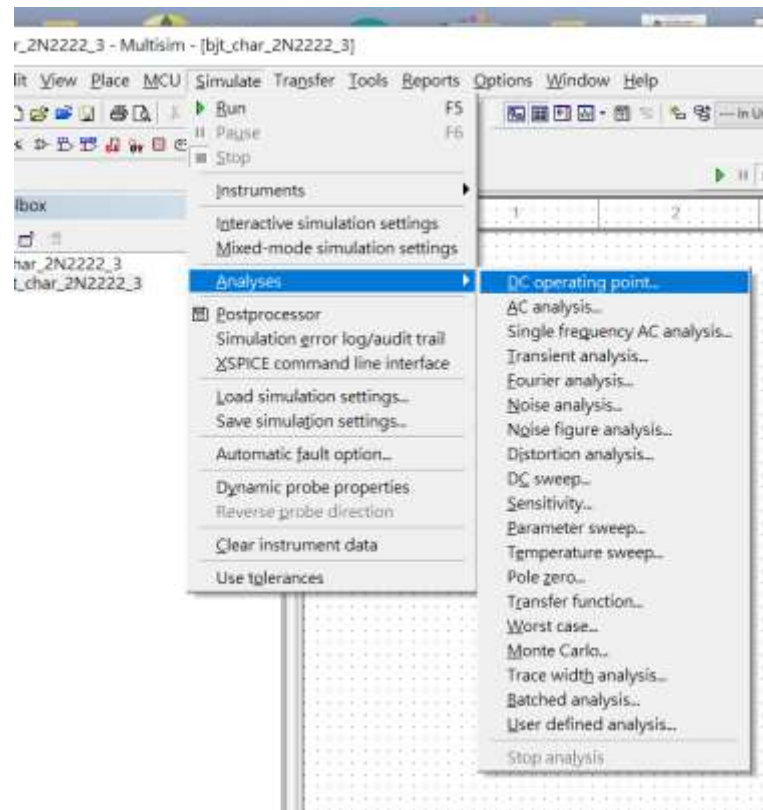


圖 6-6-2 操作程序

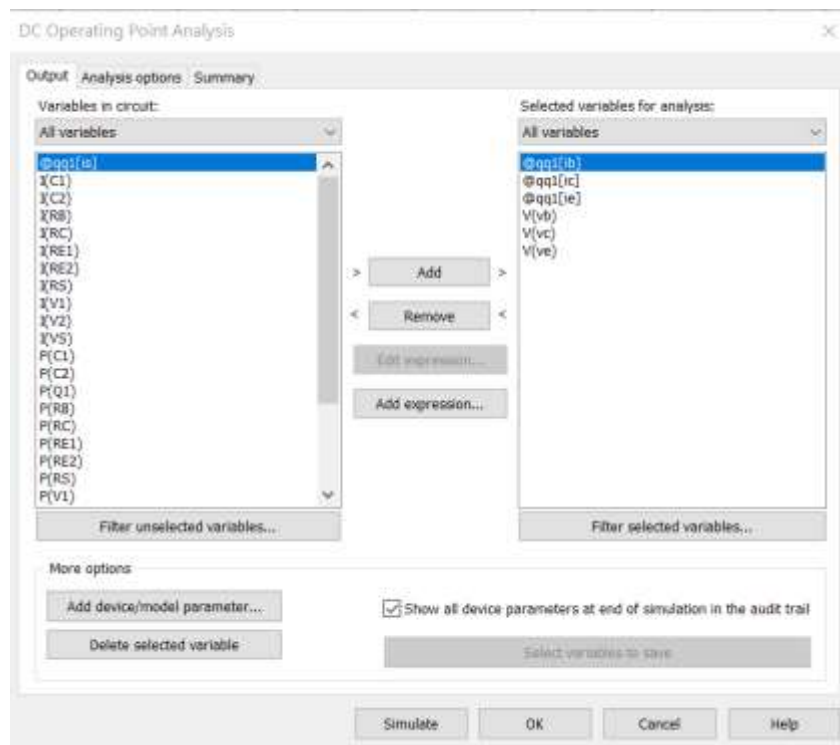


圖 6-6-3 選擇變量 ib, ic, ie, Vb, Vc, Ve

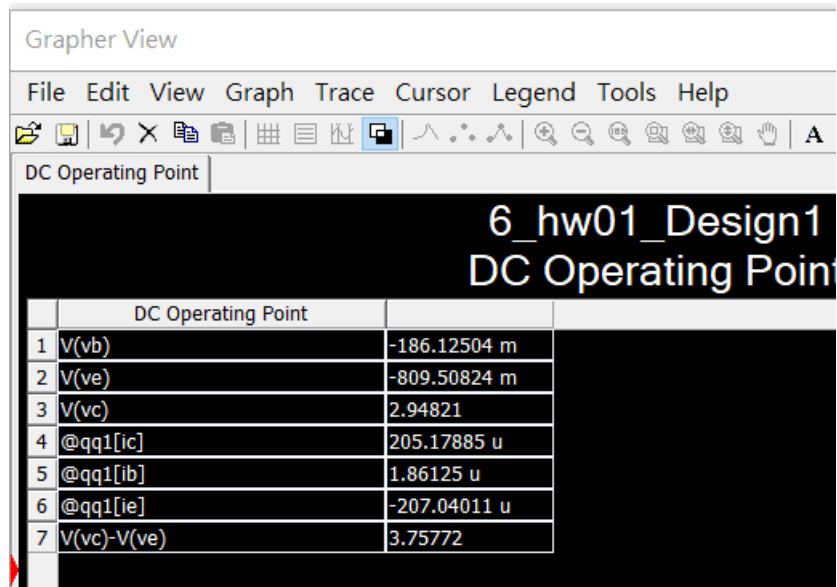


圖 6-6-4  $V_{CEQ} = V_c - V_e = 3.75V$ ,  $\beta = I_{CQ} / I_{BQ} = 205.17 / 1.86 = 110.3$

- 使用示波器顯示 V1 與 VC 之波形，並連接相關接點如上電路圖

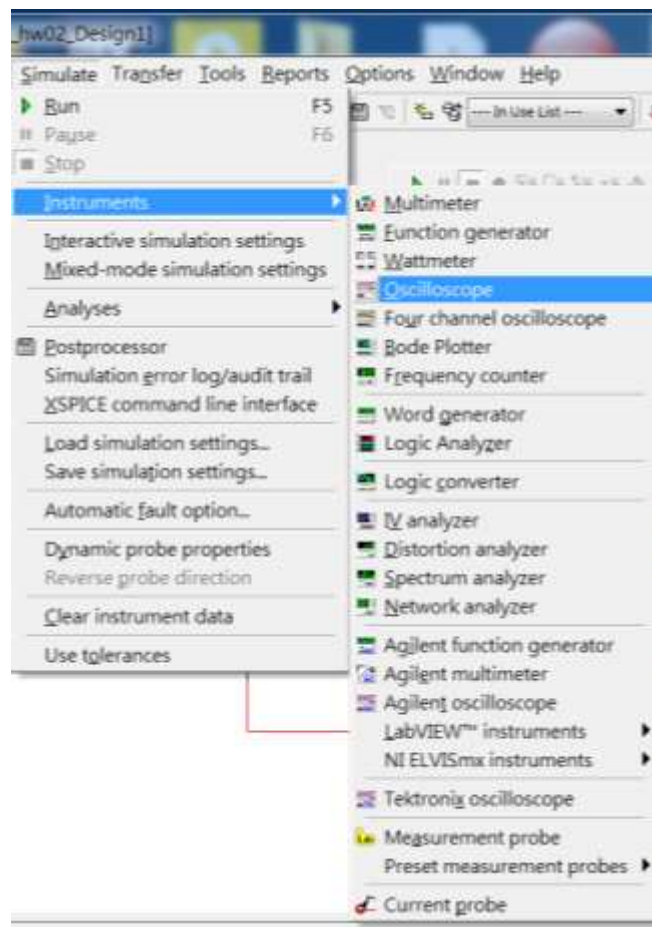


圖 6-6-5

Run → Stop



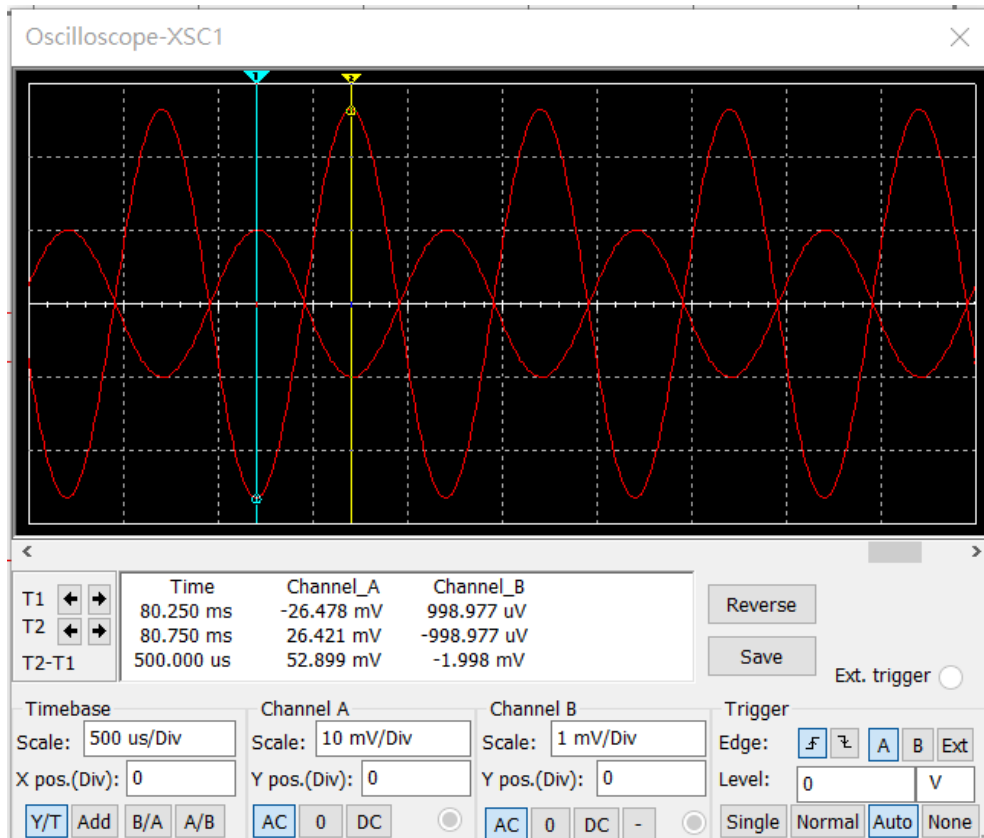



圖 6-6-6 Channel A  $V_C$  p-p = -26.478 ~ 26.421 mV = 52.899 mv,  
Channel B  $V_s$  p-p = -998.977 ~ 998.977 uV = 2mv

放大率計算  $|A_v| = |V_C| / |V_s| = 52.899/2 = 26.44 \ll R_C / R_{E1} = 10K/.24K = 41.66$

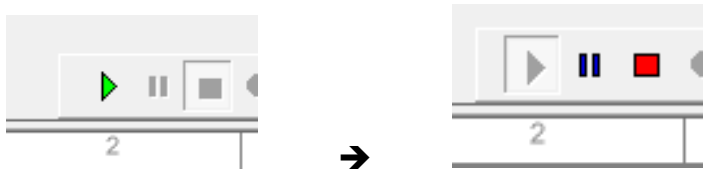

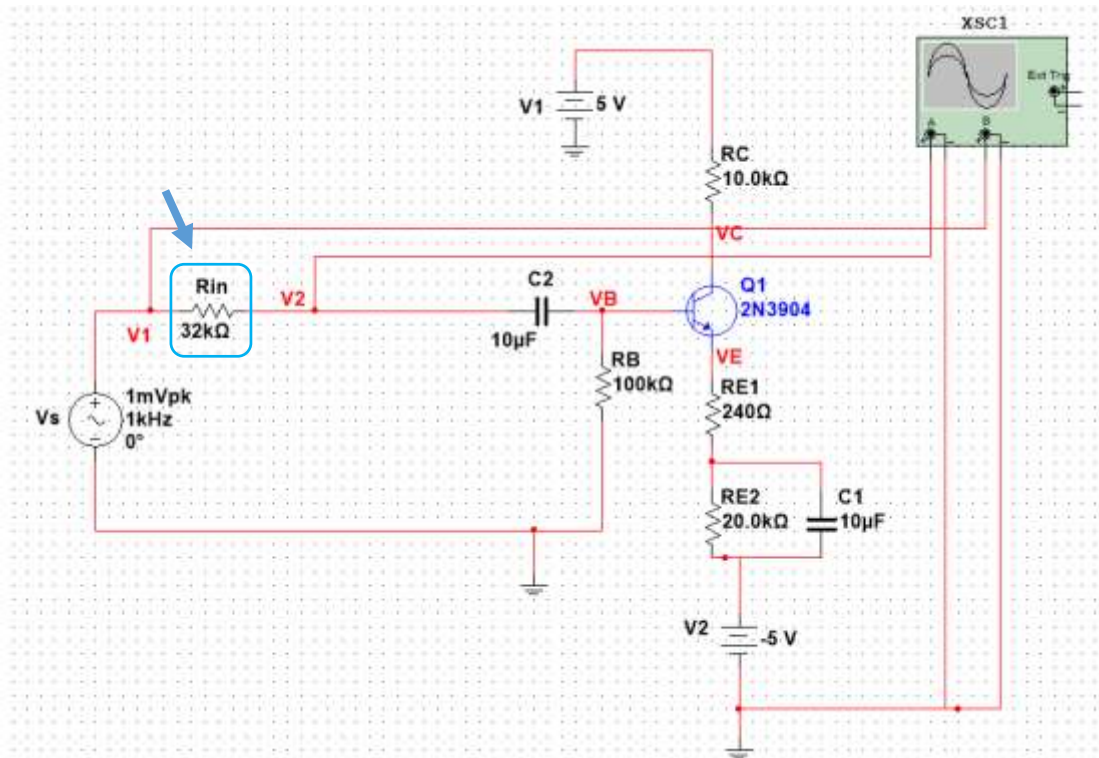

Oscilloscope-XSC1

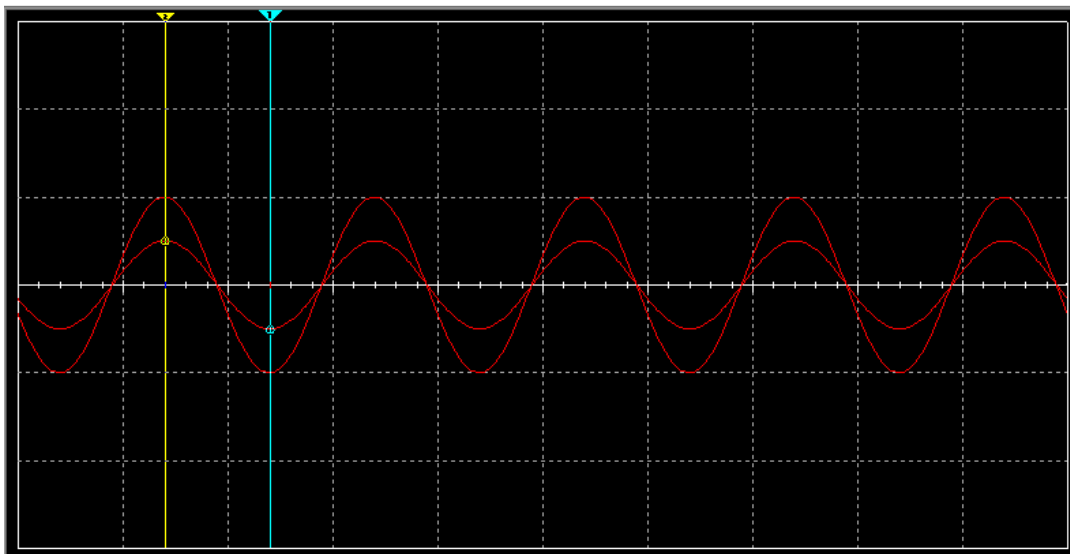

	Time	Channel_A	Channel_B
T1	28.751 ms	-500.048 uV	-999.845 uV
T2	28.251 ms	500.098 uV	999.845 uV
T2-T1	-500.000 us	1.000 mV	2.000 mV

Timebase: Scale: 500 us/Div  
 Channel A: Scale: 1 mV/Div  
 Channel B: Scale: 1 mV/Div  
 Trigger: Edge: f, A, B, Ext; Level: 0 V; Mode: Auto

圖 6-6-7 設定輸入電阻  $R_{in} = 32K$ ，使得  $|V_{2p-p}| / |V_{1p-p}| = 1mV/2mV = 0.5$

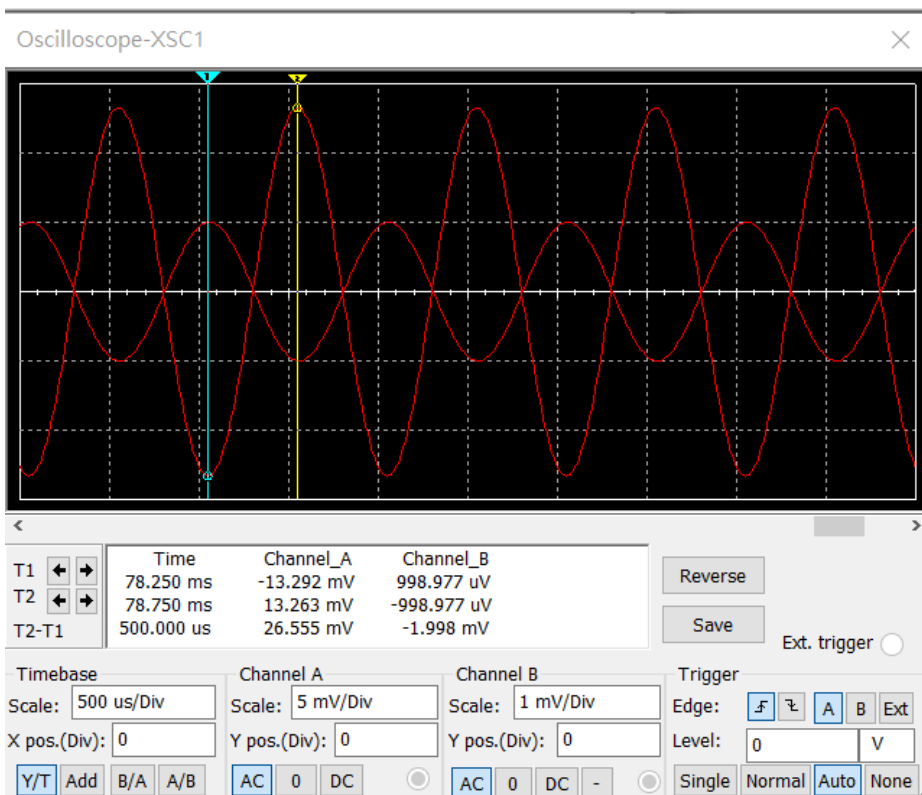
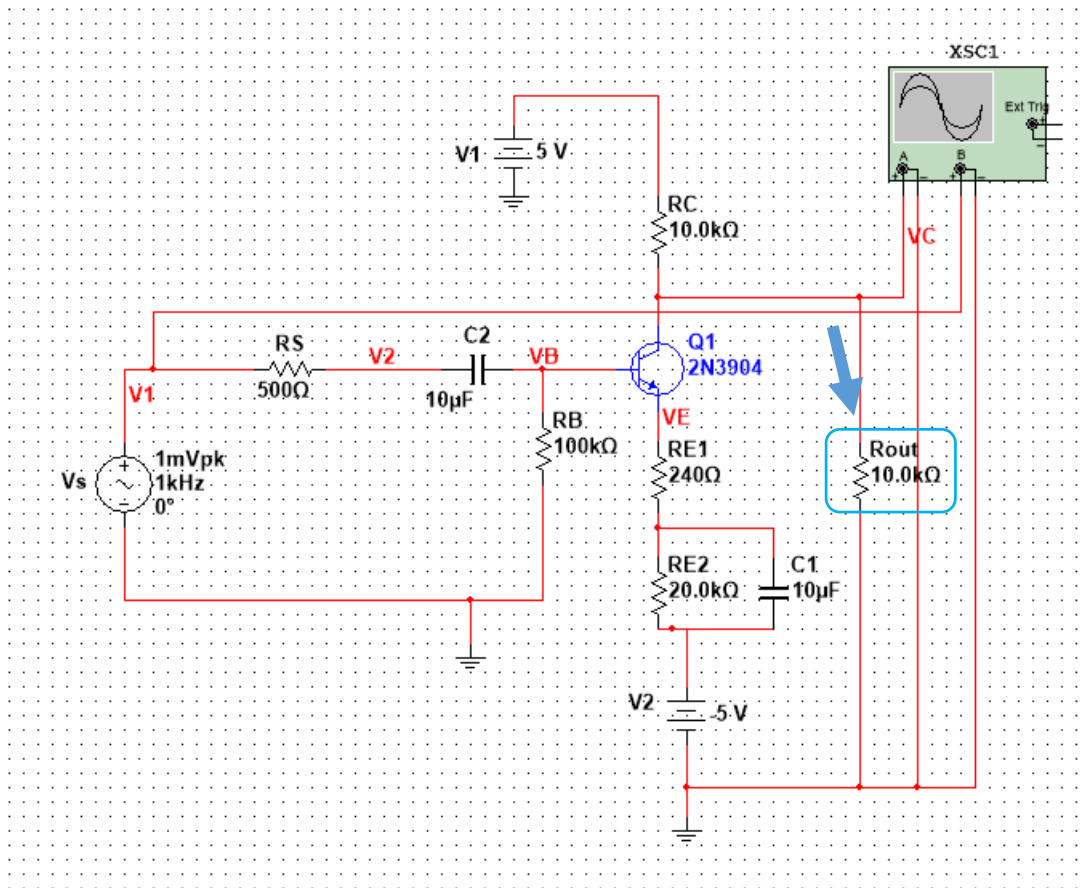


圖 6-6-8 設定輸出電阻  $R_{out} = 10.0K$ ，使得  $|V_{Rc p-p}| / |V_{1 p-p}| = 26.5mv / 2mv = 13.25$  是原來 26.44 (圖 A-6)之半值。

理論值計算如下:

1) 電流放大率  $\Rightarrow \beta = \frac{I_{CQ}}{I_{BQ}} = 205.17/1.86 = 110.3$  (由圖 6-6-4 得知)

2) BE 導通電阻

$$r_b = r_\pi = \frac{\beta V_T}{I_{CQ}} = 110.3 * 0.026 / 205.17 * 10^{-6} = 13.98 \text{K}\Omega$$

3)  $R_{bb} = 100 \text{K}\Omega$

$$\begin{aligned} \text{輸入電阻} \Rightarrow R_{in} &= \frac{V_i}{i_s} = R_{bb} // (r_\pi + (1 + \beta)R_{e1}) \\ &= 100 // (13.98 + (1 + 110.3) * 0.24) \\ &= 100 // 40.69 = 28.92 \text{K}\Omega \end{aligned}$$

4) 輸出電阻  $\Rightarrow R_{out} = R_C = 10 \text{K}\Omega$

$$\begin{aligned} \text{5) 電壓放大率} \Rightarrow A_v &= \frac{V_o}{V_s} = \frac{V_o}{V_i} * \frac{V_i}{V_s} = \frac{-i_c * R_C}{i_b * (r_\pi + (1 + \beta)R_{e1})} * \frac{R_{in}}{R_{in} + R_s} \\ &= \frac{-\beta * R_C}{r_\pi + (1 + \beta)R_{e1}} * \frac{R_{in}}{R_{in} + R_s} \\ &= \frac{-110.3 * 10}{13.98 + (1 + 110.3) * 0.24} * \frac{28.92}{28.92 + 0.5} = -26.64 \end{aligned}$$

## 二、作業:

6-1: 參考圖 6-7 共射放大電路模擬圖:

- 找出 Q-point 的  $V_{CEQ}$ 、 $I_{BQ}$  與  $I_{CQ}$ ， $\beta = I_{CQ} / I_{BQ} = ?$
- 計算  $A_v = ?$  比較理論值與模擬電路輸出入  $V_{p-p}$  波形比率值。
- 計算輸出入電阻  $R_{in}$ ， $R_{out}$ ，並修改該模擬圖 6-7 驗證該輸出入電阻計算值是否相近。

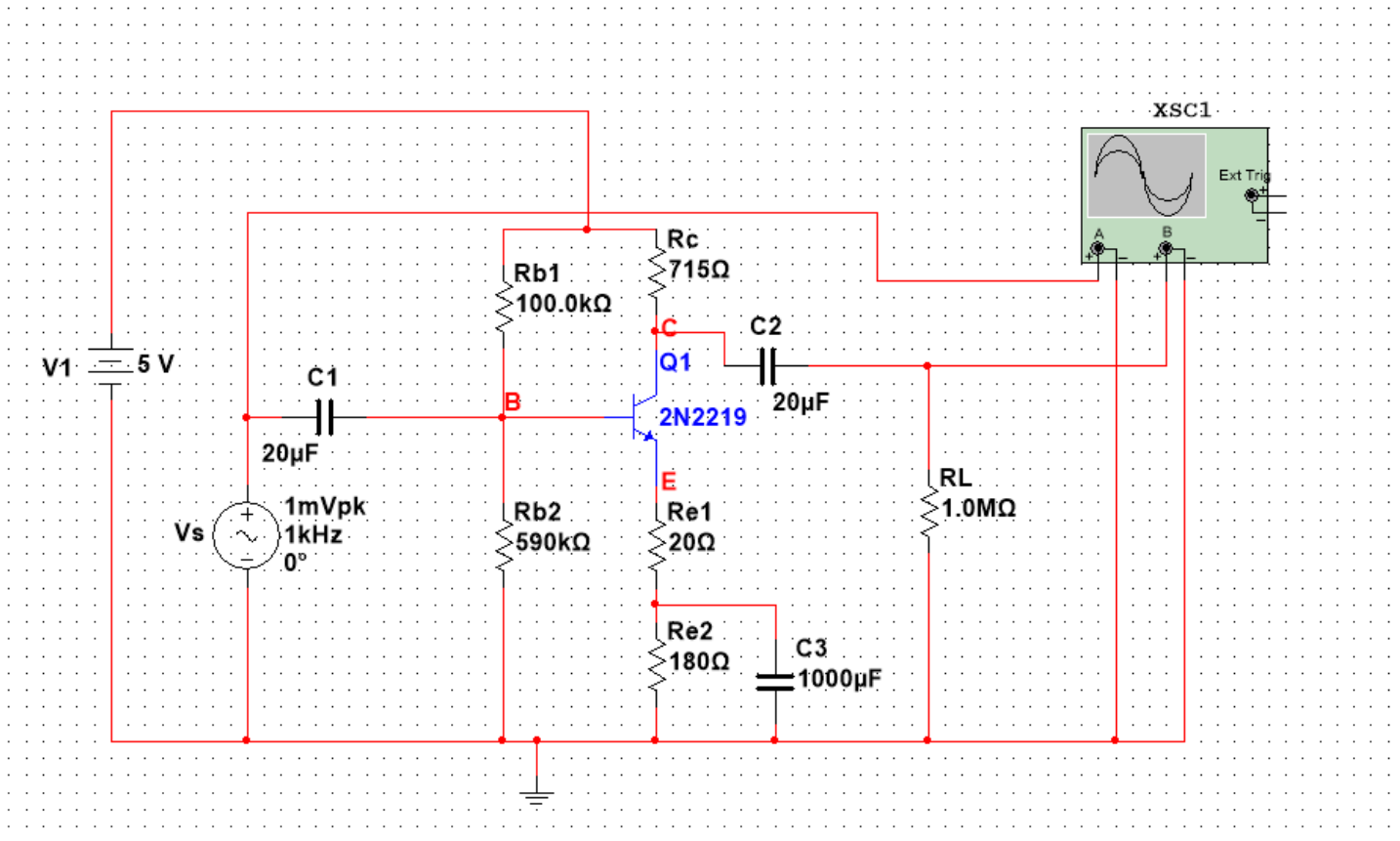


圖 6-7 作業電路圖

6-2: 續上題，可能因電容選擇不當(如  $C_1, C_2 = 10\mu F$  修改為  $0.1\mu F$ )，請選擇適當電容使得  $|A_v|$  之值增加並接近期望值  $R_c / R_{E1} = 41.66$ ，並以 MultiSim ver. 12 驗證  $|A_v| = ?$