

第 7 講: BJT 電晶體共集(Common Collector)放大電路

參考文獻與網頁:

[1]蕭敏學，大學電子學實習(一):電子電路分析篇，台科大圖書，2013

[2]Common Collector Amplifire,

<https://www.electronics-tutorials.ws/amplifier/common-collector-amplifier.html>

[3]Basic BJT Amplifier,

<http://cdcpc.ce.ncu.edu.tw/classes/EEShortversion/Elect/Ch6%20Basic%20BJT%20Amplifiers.pdf>

一、電路分析，請參考[1]~[3]

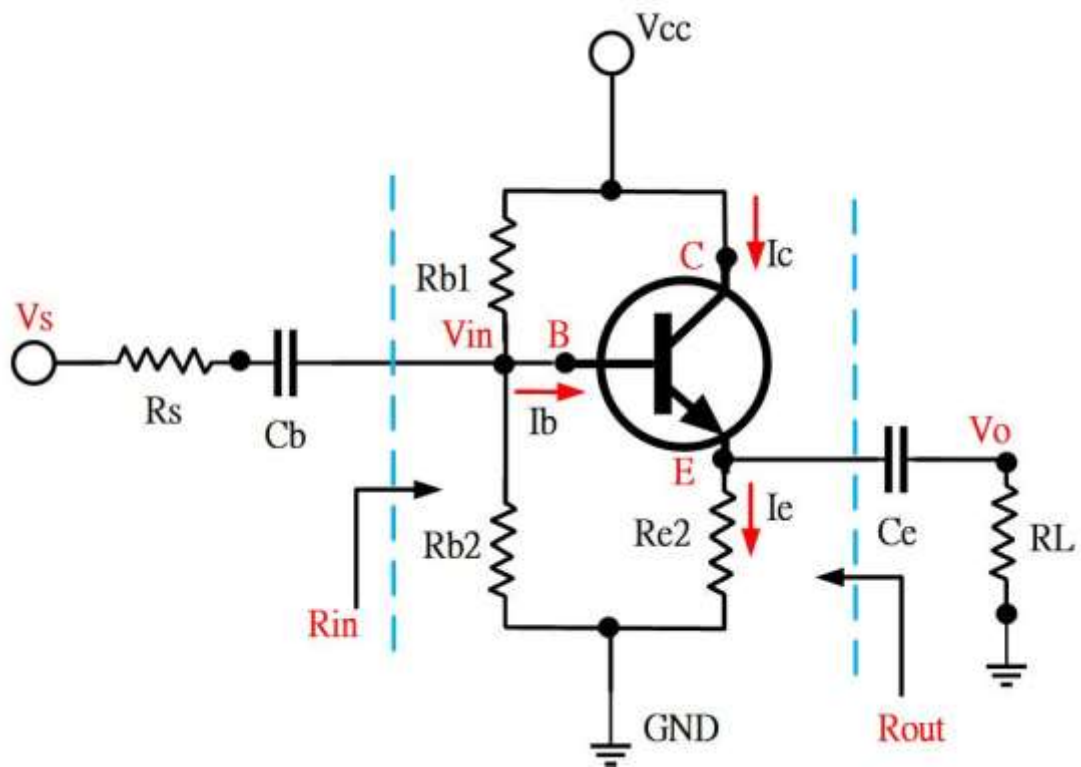


圖 7-1 BJT 電晶體共集電路[2]

● 電壓放大率:

$$A_v = \frac{V_{out}}{V_{in}} = \frac{(1+\beta)(R_{e2} // R_L)}{R_{b1} // R_{b2} // (r_{\pi} + (1+\beta)(R_{e2} // R_L))} = \frac{(1+\beta)(R_{e2} // R_L)}{r_{\pi} + (1+\beta)(R_{e2} // R_L)} \cong 1 \quad (7.1)$$

- 電流放大率:

$$A_i = \frac{I_e}{I_b} = (1 + \beta) , \quad \beta = \frac{I_{CQ}}{I_{BQ}} \quad (7.2)$$

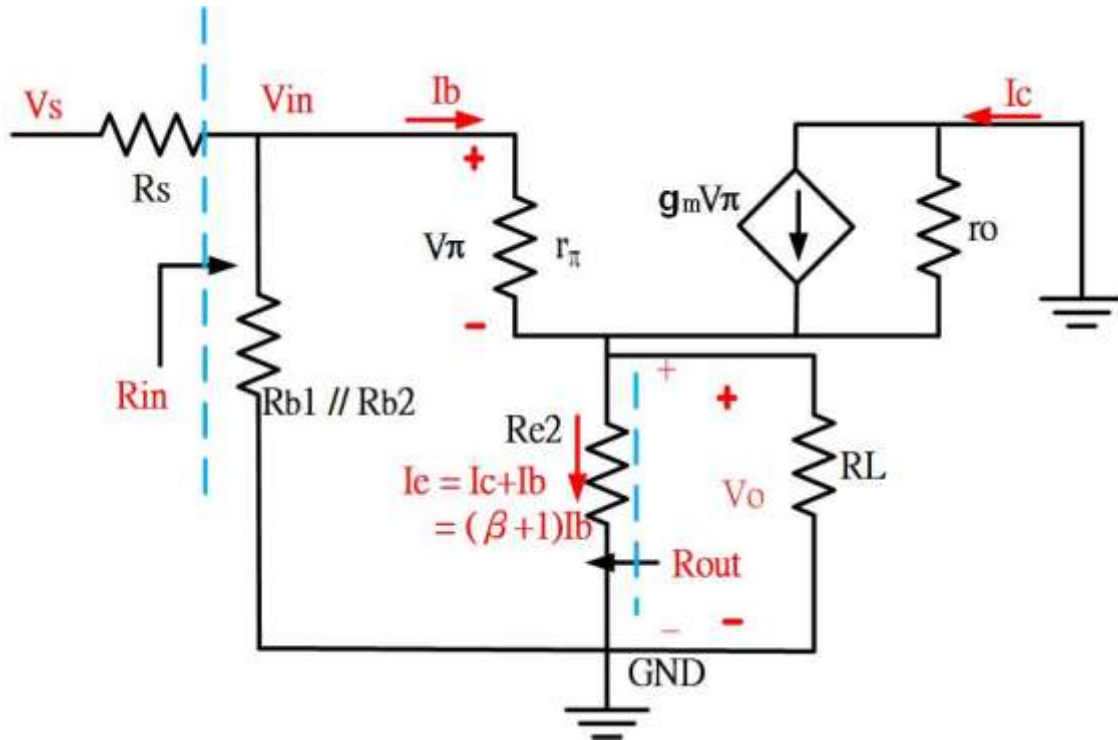


圖 7-2 BJT 電晶體共集電路小訊號模型[3]

- 輸入電阻:

$$R_{in} = R_{b1} // R_{b2} // (r_{\pi} + (1 + \beta)(r_o // R_{e2} // R_L)) \leq R_{b1} // R_{b2} // (r_{\pi} + (1 + \beta)(R_{e2} // R_L)) \quad (7.3)$$

$$r_{\pi} = \frac{\beta V_T}{I_{CQ}} \quad (7.4)$$

熱電壓(Thermal Voltage):

$$V_T = 25 \times 10^{-3} \text{ V (室溫)}$$

- 輸出電阻:

$$R_{out} = \left(\frac{R_S // R_{b1} // R_{b2} + r_{\pi}}{1 + \beta} \right) // r_o // R_{e2} \leq \left(\frac{R_S // R_{b1} // R_{b2} + r_{\pi}}{1 + \beta} \right) // R_{e2} \quad (7.5)$$

● BJT 電晶體共集電路小訊號等效電路範例 1[3]

Example 4.10 Objective: Calculate the small-signal voltage gain of an emitter-follower circuit.

For the circuit shown in Figure 4.44, assume the transistor parameters are: $\beta = 100$, $V_{BE(on)} = 0.7\text{ V}$, and $V_A = 80\text{ V}$.

Solution: The dc analysis shows that $I_{CQ} = 0.793\text{ mA}$ and $V_{CEQ} = 3.4\text{ V}$. The small-signal hybrid- π parameters are determined to be

$$r_{\pi} = \frac{V_T \beta}{I_{CQ}} = \frac{(0.026)(100)}{0.793} = 3.28\text{ k}\Omega$$

$$g_m = \frac{I_{CQ}}{V_T} = \frac{0.793}{0.026} = 30.5\text{ mA/V}$$

and

$$r_o = \frac{V_A}{I_{CQ}} = \frac{80}{0.793} \cong 100\text{ k}\Omega$$

We may note that

$$R_{ib} = 3.28 + (101)(100 \parallel 2) = 201\text{ k}\Omega$$

and


$$R_i = 50 \parallel 50 \parallel 201 = 22.2\text{ k}\Omega$$

The small-signal voltage gain is then

$$A_v = \frac{(101)(100 \parallel 2)}{3.28 + (101)(100 \parallel 2)} \cdot \left(\frac{22.2}{22.2 + 0.5} \right)$$

or

$$A_v = +0.962$$

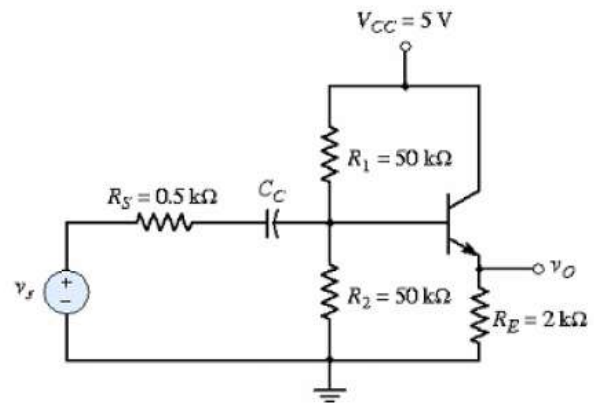

例題 2: 參考圖 7-3-1 共集放大電路模擬圖:

- 找出 Q-point 的 V_{CEQ} 、 I_{BQ} 與 I_{CQ} ， $\beta = I_{CQ} / I_{BQ} = ?$
- 計算輸出入電阻 R_{in} 、 R_{out} ，並修改該電路模擬圖 7-3-1 驗證該輸出入電阻計算值是否相近。
- 計算 $A_v = ?$ 比較理論值與模擬電路輸出入 V_{p-p} 波形比率值。

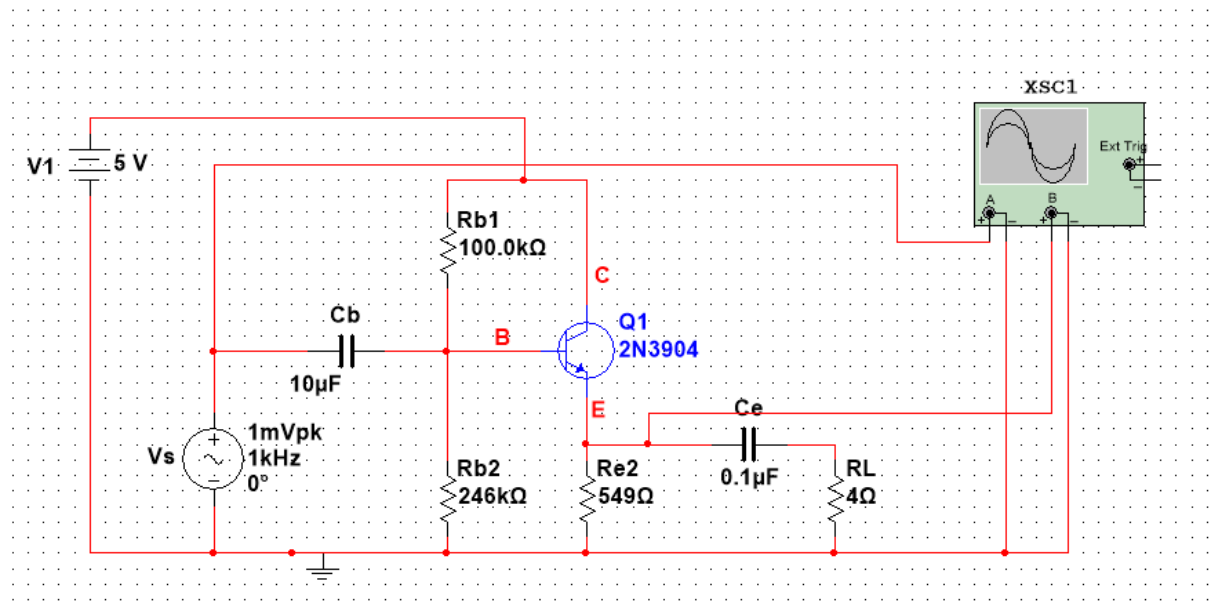


圖 7-3-1 共集放大電路模擬圖

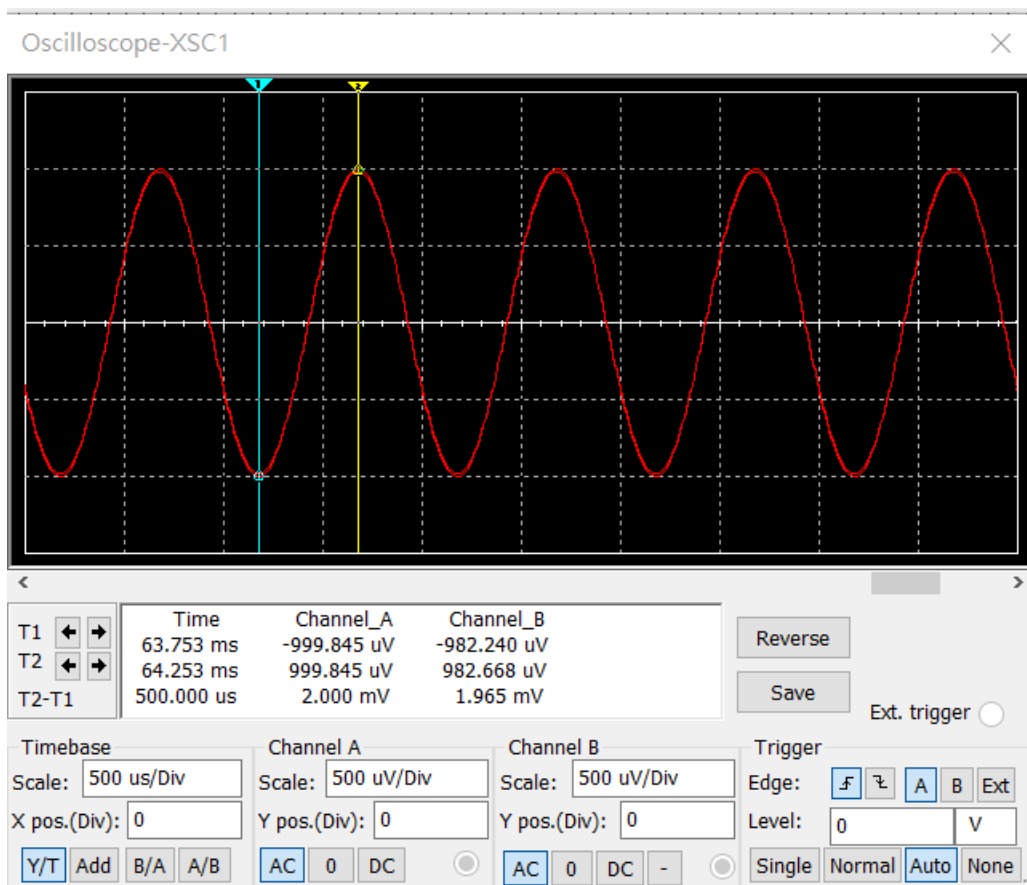


圖 7-3-2 輸入端 Vs 輸入波形與電阻 Re2 端輸出波形(因兩者同相位，波形重疊), $A_v = 1.965/2 = 0.9825$

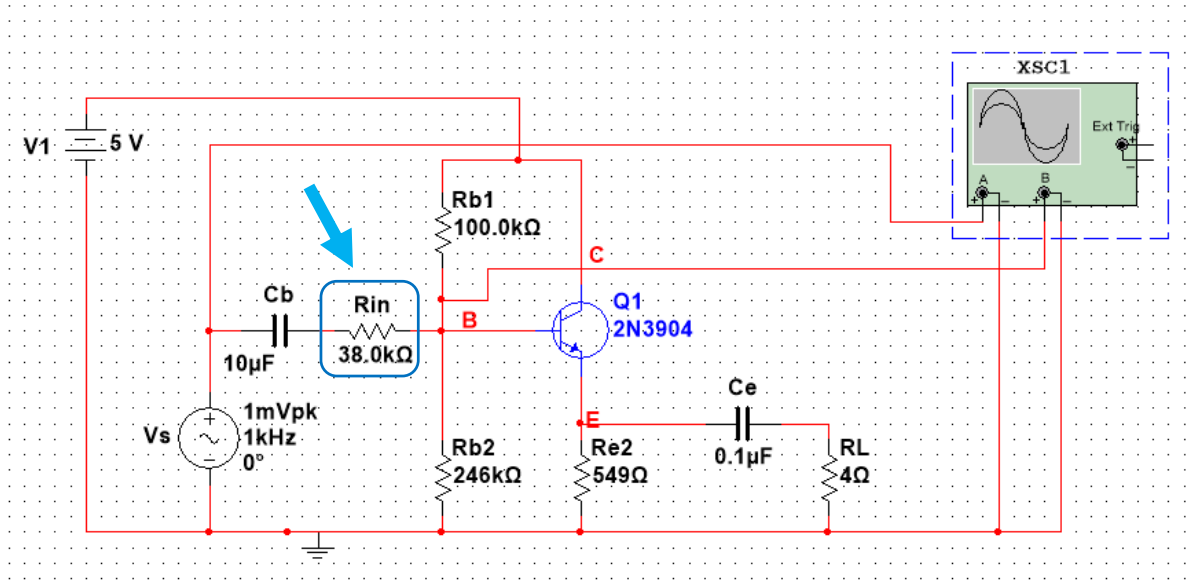


圖 7-3-3 輸入電阻 $R_{in} = 38.0\text{ k}\Omega$

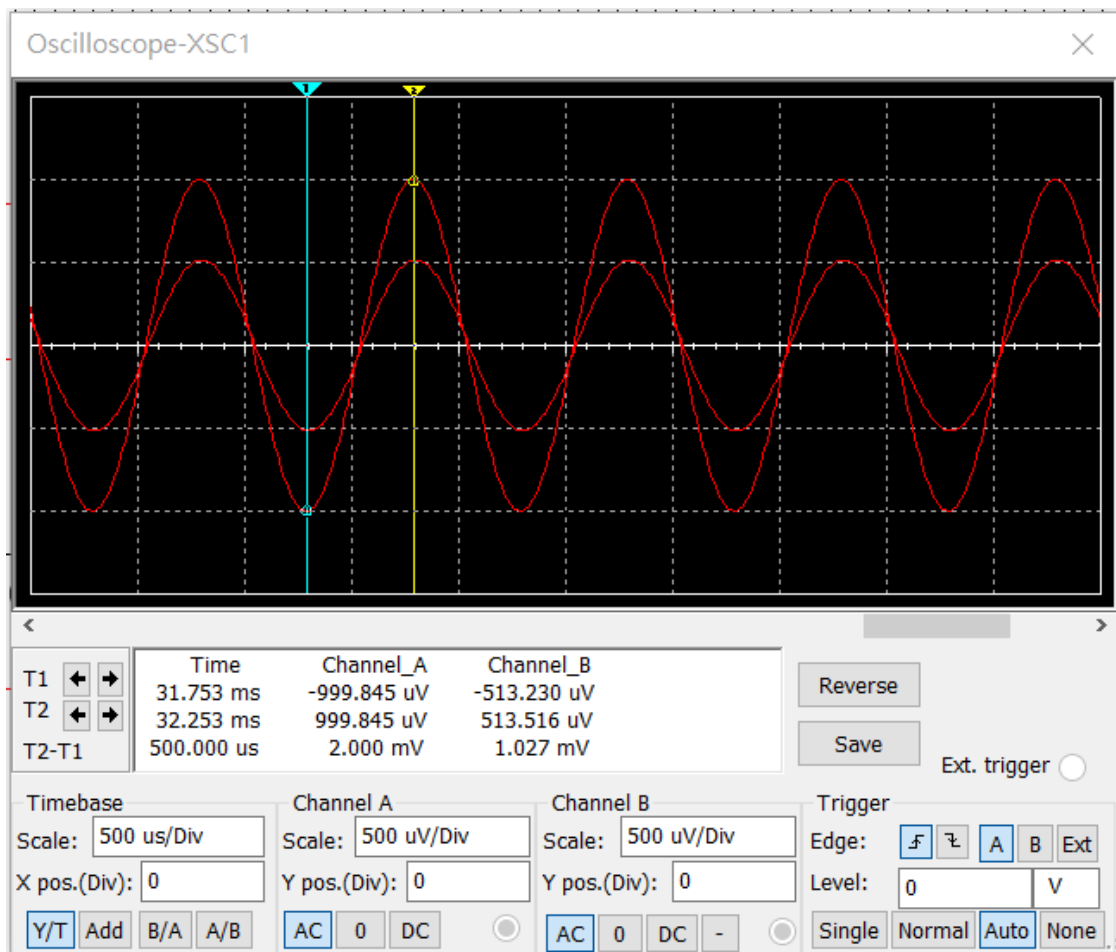


圖 7-3-4 VB 端電壓波形為輸入波形 Vs 的半值

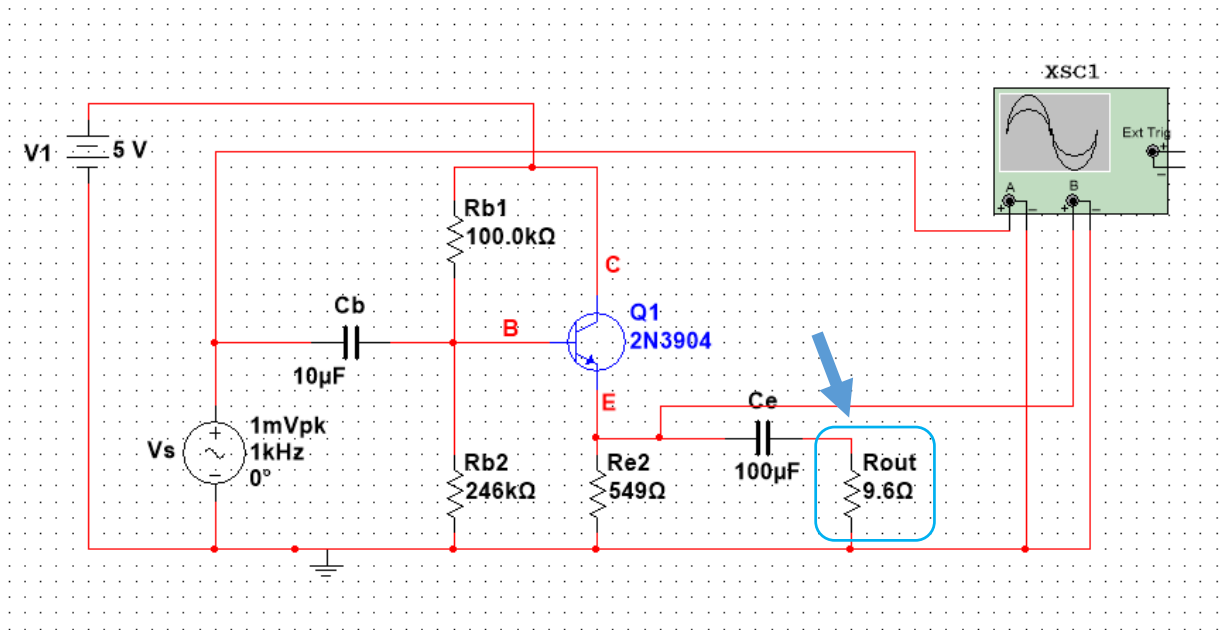


圖 7-3-5 輸出電阻 $R_{out} = 9.6 \Omega$

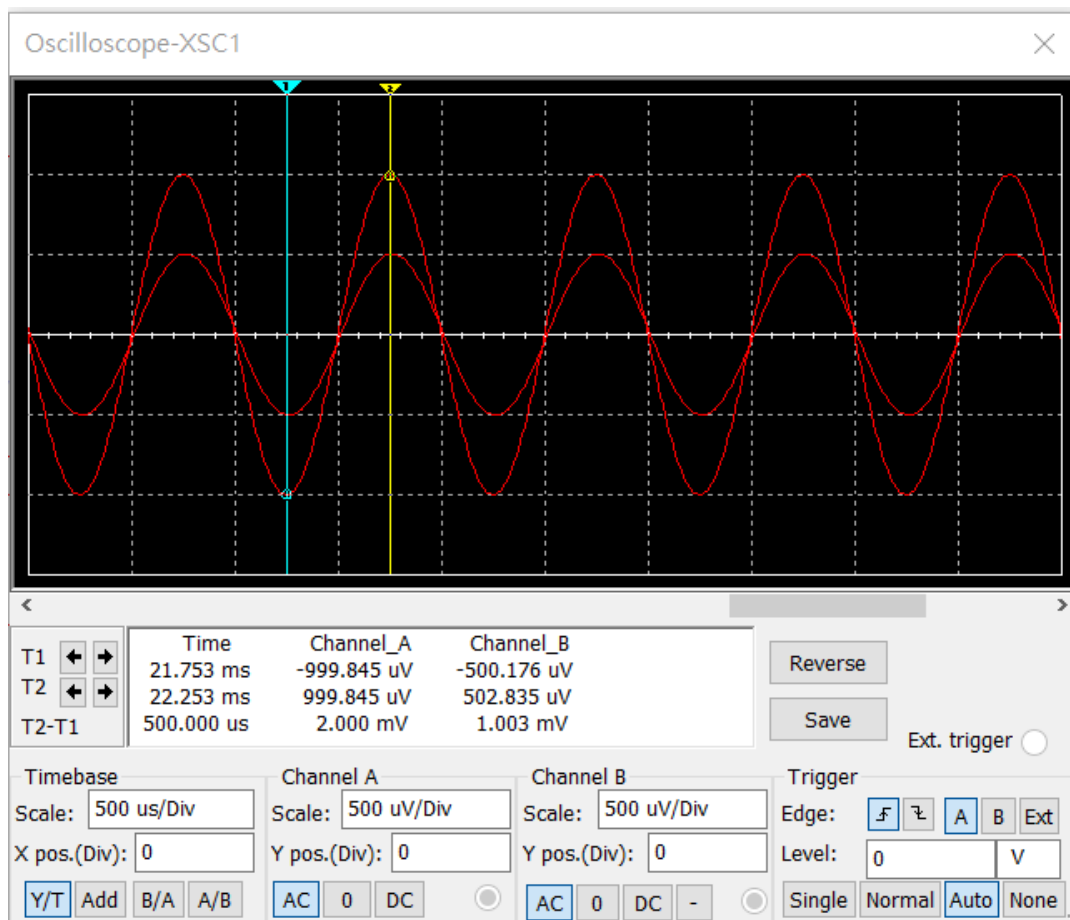


圖 7-3-6 電阻 R_{e2} 端電壓波形為輸入波形 V_s 的半值

Grapher View

DC Operating Point		
1	V(e)	1.56025
2	V(b)	2.25271
3	V(c)	5.00000
4	V(c)-V(e)	3.43975
5	@qq1[ic]	2.82498 m
6	@qq1[ib]	18.32278 u
7	@qq1[ie]	-2.84331 m

圖 7-3-7 $V_{CEQ} = V_c - V_e = 3.44V$, $\beta = I_{CQ} / I_{BQ} = 2.824m / 18.32u = 154.14$

● 輸入電阻:

熱電壓(Thermal Voltage): $V_T = 25 \times 10^{-3} V$ (室溫)

$$r_{\pi} = \frac{\beta V_T}{I_{CQ}} = \frac{154 * 0.026}{2.824 * 10^{-3}} = 1.417 \text{ K}\Omega$$

$$\begin{aligned} R_{in} &= R_{b1} // R_{b2} // (r_{\pi} + (1 + \beta)(r_o // R_{e2} // R_L)) \\ &\leq R_{b1} // R_{b2} // (r_{\pi} + (1 + \beta)(R_{e2} // R_L)) \\ &= 100K // 246K // (1.417K + (1 + 154)(549 // 4)) = 1,976 \text{ }\Omega \end{aligned}$$

(此答案與圖 7-3-3 輸入電阻 $R_{in} = 38.0 \text{ K}\Omega$ 落差明顯)

若考量 $C_e = 0.1\mu F$ 電容效應(即容抗 $1/j\omega C$)，則上面公式需修改為

$$\begin{aligned} R_{in} &= R_{b1} // R_{b2} // (r_{\pi} + (1 + \beta)(r_o // R_{e2} // (R_L + 1/j\omega C))) \\ &\leq R_{b1} // R_{b2} // (r_{\pi} + (1 + \beta)(R_{e2} // (R_L + 1/j\omega C))) \\ &= 100K // 246K // (1.417K + (1 + 154)(549 // (4 \\ &\quad + \frac{1}{j * 1000 * 2\pi * 0.1 * 10^{-6}}))) \\ &= 100K // 246K // (1.417K + (1 + 154)(549 // (4 - 1.59 * 10^3 j)) \\ &= 38.52K \angle - 8.69^\circ \Omega \end{aligned}$$

(此答案與圖 7-3-3 輸入電阻 $R_{in} = 38.0 \text{ K}\Omega$ 相差甚小)

- 輸出電阻:

$$\begin{aligned}
 R_{out} &= \left(\frac{R_S // R_{b1} // R_{b2} + r_{\pi}}{1 + \beta} \right) // r_o // R_{e2} \\
 &\leq \left(\frac{R_S // R_{b1} // R_{b2} + r_{\pi}}{1 + \beta} \right) // R_{e2} \\
 &= \frac{0 + 1417}{155} // 549 = 9.0 \Omega
 \end{aligned}$$

(此答案與 圖 7-3-5 輸出電阻 $R_{out} = 9.6 \Omega$ 相差不遠)

- 電壓放大率:

$$A_v = \frac{V_{out}}{V_{in}} = \frac{(1 + \beta)(R_{e2} // R_L)}{R_{b1} // R_{b2} // (r_{\pi} + (1 + \beta)(R_{e2} // R_L))} = \frac{(1 + \beta)(R_{e2} // R_L)}{R_{in}} = \frac{(1 + \beta)(R_{e2} // R_L)}{r_{\pi} + (1 + \beta)(R_{e2} // R_L)} \cong 1$$

若不考量 $C_e = 0.1 \mu F$ 電容效應(即容抗 $1/j\omega C$)，電壓放大率遠小於 1，如下計算:

$$A_v = \frac{V_{out}}{V_{in}} = \frac{(1 + \beta)(R_{e2} // R_L)}{r_{\pi} + (1 + \beta)(R_{e2} // R_L)} = \frac{(1 + 154) * (549 // 9.6)}{2032} = 0.3028$$

若考量 $C_e = 0.1 \mu F$ 與 $C_b = 10 \mu F$ 電容效應，電壓放大率接近於 1，如下計算:

$$\begin{aligned}
 A_v &= \frac{V_{out}}{V_{in}} = \frac{(1 + \beta)(R_{e2} // (R_L + 1/j\omega C_e))}{r_{\pi} + (1 + \beta)(R_{e2} // (R_L + 1/j\omega C_e)) + 1/j\omega C_b} \\
 &= \frac{(1 + 154)(549 // (4 - 1.59 * 10^3 j))}{1417 + (1 + 154)(549 // (4 - 1.59 * 10^3 j)) - 15.91 j} \\
 &= 0.9835 \angle -0.3131^\circ
 \end{aligned}$$

(此理論值與圖 7-3-2 $A_v = 0.9825$ 非常接近)

二、作業:

作業 7-1: 共集電路模擬圖如圖 7-4 ,

- 找出 Q-point 的 V_{CEQ} 、 I_{BQ} 與 I_{CQ} , $\beta = I_{CQ} / I_{BQ} = ?$
- 計算輸出入電阻 R_{in} , R_{out} , 並修改該電路模擬圖 7-4 驗證該輸出入電阻與理論值是否相近。
- 計算 $A_v = ?$ 比較理論值與模擬電路輸出入 V_{p-p} 波形比率值。

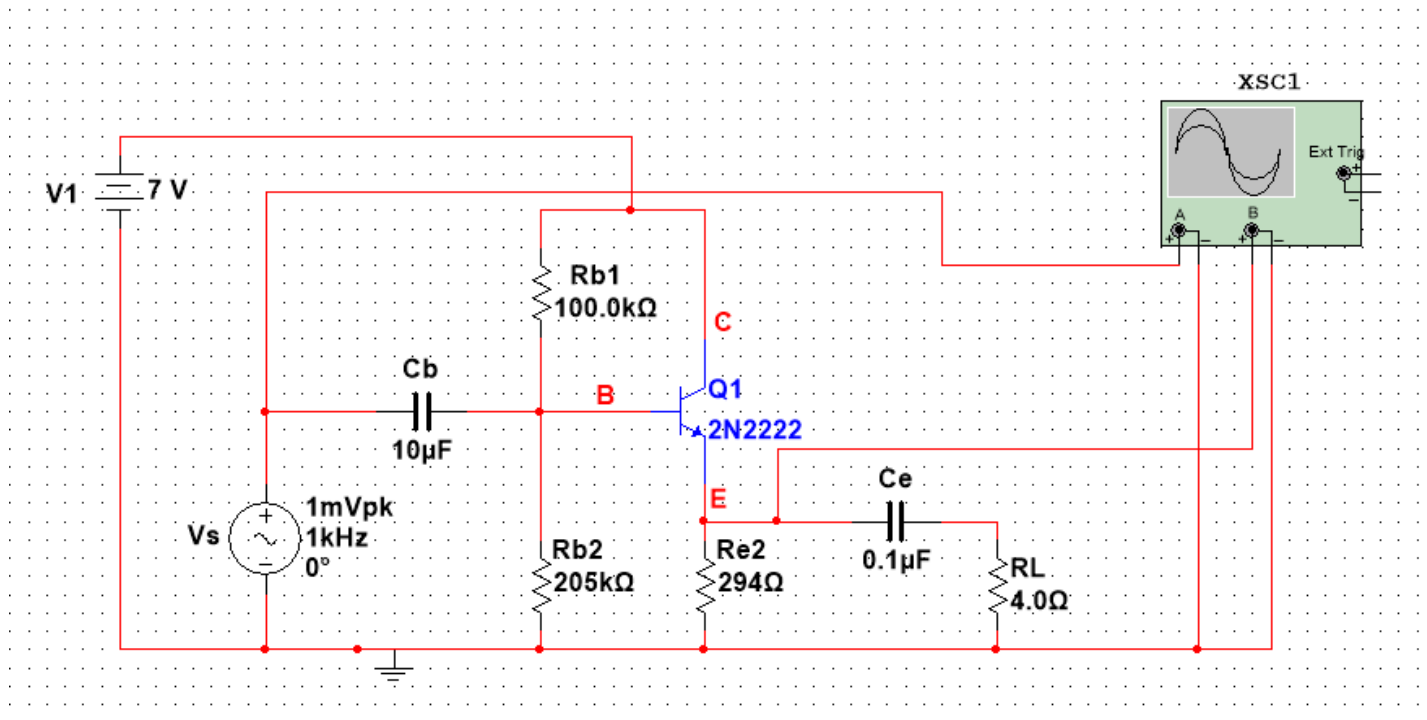


圖 7-4 作業 7-1 共集電路模擬圖

作業 7-2: 續上題,

- 計算輸出入電阻 R_{in} , R_{out} , 與電路模擬圖 7-4 有極大的差異, 請問該如何修改。
- 在模擬圖 7-3-5 驗證 $R_{out} = 9.6\Omega$, 為何 $C_e = 0.1\mu f$ 改為 $C_e = 100\mu f$? 請說明。

附錄: 計算 Rin 與 Av 的 Matlab 程式

```
function result = calpara(a, b)
    result = a*b/(a + b);
end
```

```
% 計算 Rin
```

```
Rb1 = 100e3;
Rb2 = 246e3;
Ce = 0.1e-6;
f = 1000;
beta = 154;
Re2 = 549;
RL = 4;
rpi = 1417;
```

```
%不考量Ce容抗之Rin計算
```

```
a = rpi + (1+beta)*calpara(Re2, RL);
b = calpara(Rb1, Rb2);
Rin_1 = calpara(a, b)
```

```
%考量Ce容抗之Rin計算
```

```
a = rpi + (1+beta)*calpara(Re2, RL-i/(2*pi*f*Ce))
Rin_2 = calpara(a, b)
abs(Rin_2)
angle(Rin_2)*360/(2*pi)
```

```
% 計算 Av
```

```
Rb1 = 100e3;
Rb2 = 246e3;
Ce = 0.1e-6;
f = 1000;
beta = 154;
Re2 = 549;
RL = 4;
rpi = 1417;
```

```
Cb = 10e-6;
```

```
%不考量Cb,Ce容抗之Av計算
```

```
a = rpi + (1+beta)*calpara(Re2, RL);
```

```
Rbb = calpara(Rb1, Rb2);
```

```
Rin_1 = a
```

```
Av_1 = (1+beta)*calpara(Re2, RL)/Rin_1
```

```
%考量Cb,Ce容抗之Av計算
```

```
a2 = rpi+ (1+beta)*calpara(Re2, RL-i/(2*pi*f*Ce))
```

```
Rin_2 = a2 -i/(2*pi*f*Cb)
```

```
Av_2 = (1+beta)*calpara(Re2, RL-i/(2*pi*f*Ce))/Rin_2
```

```
abs(Av_2)
```

```
angle(Av_2)*360/(2*pi)
```